

## Processor Architecture II: Logic Design

Dr. Steve Goddard  
[goddard@cse.unl.edu](mailto:goddard@cse.unl.edu)

<http://cse.unl.edu/~goddard/Courses/CSCE230J>

## Giving credit where credit is due

- Most of slides for this lecture are based on slides created by Dr. Bryant, Carnegie Mellon University.
- I have modified them and added new slides.

2

## Overview of Logic Design

### Fundamental Hardware Requirements


- Communication
  - How to get values from one place to another
- Computation
- Storage

### Bits are Our Friends

- Everything expressed in terms of values 0 and 1
- Communication
  - Low or high voltage on wire
- Computation
  - Compute Boolean functions
- Storage
  - Store bits of information

3


## Digital Signals

 


- Use voltage thresholds to extract discrete values from continuous signal
- Simplest version: 1-bit signal
  - Either high range (1) or low range (0)
  - With guard range between them
- Not strongly affected by noise or low quality circuit elements
  - Can make circuits simple, small, and fast

4

## Computing with Logic Gates

 


 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs
  - With some, small delay



5

## Combinational Circuits

 


### Acyclic Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (after some delay) Boolean functions of primary inputs

6

## Bit Equality

 


- Generate 1 if a and b are equal

### Hardware Control Language (HCL)

- Very simple hardware description language
  - Boolean operations have syntax similar to C logical operations
- We'll use it to describe control logic for processors

7


## Word Equality

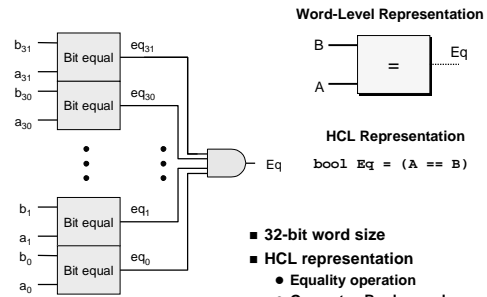

- 32-bit word size
- HCL representation
  - Equality operation
  - Generates Boolean value

8


## Bit-Level Multiplexor

 

- Control signal s
- Data signals a and b
- Output a when s=1, b when s=0

9

## Word Multiplexor

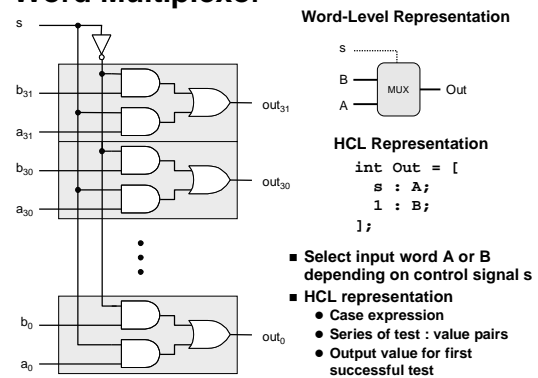


- Select input word A or B depending on control signal s
- HCL representation
  - Case expression
  - Series of test : value pairs
  - Output value for first successful test

10


## HCL Word-Level Examples

### Minimum of 3 Words

 

- Find minimum of three input words
- HCL case expression
- Final case guarantees match


### 4-Way Multiplexor

 

- Select one of 4 inputs based on two control bits
- HCL case expression
- Simplify tests by assuming sequential matching

11


## Arithmetic Logic Unit

 

- Combinational logic
  - Continuously responding to inputs
- Control signal selects function computed
  - Corresponding to 4 arithmetic/logical operations in Y86
- Also computes values for condition codes


12

## Storing 1 Bit

 


13

## Storing 1 Bit (cont.)

 


14

## Physical Analogy

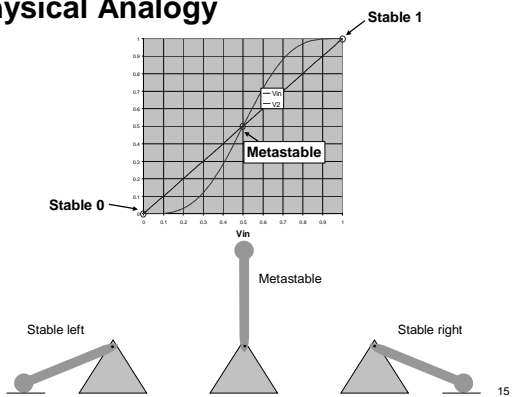


15

## Storing and Accessing 1 Bit

 


16

## 1-Bit Latch

 

17


## Transparent 1-Bit Latch

 

- When in latching mode, combinational propagation from D to Q+ and Q-
- Value latched depends on value of D as C falls

18


## Edge-Triggered Latch

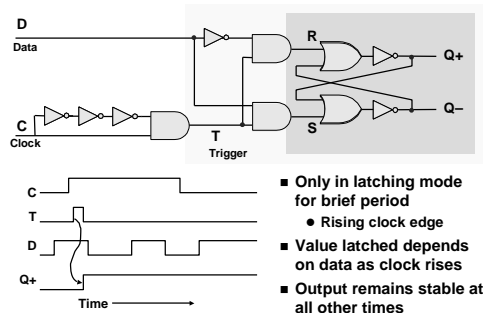

- Only in latching mode for brief period
  - Rising clock edge
- Value latched depends on data as clock rises
- Output remains stable at all other times

19


## Registers

 

- Stores word of data
  - Different from *program registers* seen in assembly code
- Collection of edge-triggered latches
- Loads input on rising edge of clock

20


## Register Operation

 


- Stores data bits
- For most of time acts as barrier between input and output
- As clock rises, loads input

21

## State Machine Example

 


 - Accumulator circuit
- Load or accumulate on each cycle



22


## Random-Access Memory

 

- Stores multiple words of memory
  - Address input specifies which word to read or write
- Register file
  - Holds values of program registers
  - %eax, %esp, etc.
  - Register identifier serves as address
    - » ID 8 implies no read or write performed
- Multiple Ports
  - Can read and/or write multiple words in one cycle
    - » Each has separate address and data input/output

23

## Register File Timing

 


### Reading

- Like combinational logic
- Output data generated based on input address
  - After some delay
 
### Writing

- Like register
- Update only as clock rises



24

## Hardware Control Language

- Very simple hardware description language
- Can only express limited aspects of hardware operation
  - Parts we want to explore and modify

### Data Types

- **bool**: Boolean
  - a, b, c, ...
- **int**: words
  - A, B, C, ...
  - Does not specify word size—bytes, 32-bit words, ...

### Statements

- `bool a = bool-expr ;`
- `int A = int-expr ;`

25

## HCL Operations

- Classify by type of value returned

### Boolean Expressions

- **Logic Operations**
  - `a && b, a || b, !a`
- **Word Comparisons**
  - `A == B, A != B, A < B, A <= B, A >= B, A > B`
- **Set Membership**
  - `A in { B, C, D }`
    - » Same as `A == B || A == C || A == D`

### Word Expressions

- **Case expressions**
  - `[ a : A; b : B; c : C ]`
  - Evaluate test expressions a, b, c, ... in sequence
  - Return word expression A, B, C, ... for first successful test

26

## Summary

### Computation

- Performed by combinational logic
- Computes Boolean functions
- Continuously reacts to input changes

### Storage

- **Registers**
  - Hold single words
  - Loaded as clock rises
- **Random-access memories**
  - Hold multiple words
  - Possible multiple read or write ports
  - Read word when address input changes
  - Write word as clock rises

27